



POPSICLE FLASHLIGHT

Name: _____

We made closed circuits when we created our modeling dough circuit and our led sculptures. This activity adds another element to a basic circuit, a switch. A switch allows you to close a circuit (have electricity flow to your bulb) or open a circuit (stop electricity from flowing to your bulb.)

KEY

Battery




Bulb



Wire



Switch

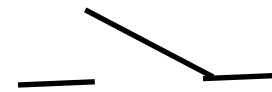

Draw the circuit you made with your Popsicle Flashlight.