

Modelling Dough Circuits

Name: _____

You will be creating a closed circuit. A closed circuit consists of a battery, wire, and bulb. When the circuit is complete electricity passes from the battery through the wire to light the bulb.

Battery



Bulb




Wire



Modeling Dough

(Draw what your creature looks like.)

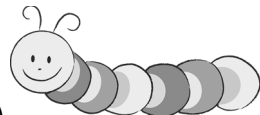

Draw a model of the circuit you will create with the modeling dough. Use the symbols given below.